

# Specifications

---

## (Single Cycle Implementation)

- **Instruction Memory**
  - Instruction Size : 16 bits
  - Address line (PC) : 10 bits
- **Data Memory**
  - Data Width : 8 bits
  - Address Width : 8 bits
- **ALU :**
  - 8bit ALU Supporting Addition, Subtraction, OR, AND, XOR and Shift operation
- **Register File :**
  - R0-R7 Registers : 8 bits each
- **Instructions Supported :**
  - ADD,ADDI,SUB,AND,OR,XOR, Shift Left, Shift Right, LOAD,LOADI,STORE, JUMP, JUMPZ, RET and NOP
- **1 Interrupt Support**

# Instruction Set


---

Instruction Type	Instructions
R-Type Instruction	ADD SUB ADDI
	OR XOR AND
	SHIFT LEFT SHIFT RIGHT
Memory Reference Instruction	LOAD LOADI STORE
Branching Instruction	JUMP JUMPZ
Miscellaneous	RET NOP

# R-Type Instruction

## R Type :-

ADD, SUB, AND, OR, XOR

 

### Field Description:

1. **Opcode** : 5 bits field:  
Bit(15:14) :10  
Bit (13:11) : **Functional Field**:- 3 bit field to describe the operation to be performed.
2. **Rd**: 3 bit field for destination register
3. **Rs2,Rs1** : 3 bit field for two source register.

FUNC. FIELD Bit (13:11)	OPERATION
000	ADD
001	SUB
011	AND
100	OR
010	XOR

# R-Type Instruction

---

## R Type :-

**ADDI** :- Add Immediate Instruction



### Field Description:

1. **Opcode** : 2 bits = 11
2. **Data MSB**: 3 bit field for immediate data MSB
3. **Rd**: 3 bit field for destination register
4. **Rs** : 3 bit field for source register.
5. **Data LSB** : 5 bit field for immediate data LSB

# R-Type Instruction

## R Type :-

SHIFTLLEFT , SHIFTRIGHT



### Field Description:


- Opcode** : 5 bits field:  
Bit(15:14) : 01  
Bit (13:11) : **Functional Field**:- 3 bit field to describe the operation to be performed.
- Rd**: 3 bit field for destination register
- Rs**: 3 bit field for two source register.
- Data** : bit field for data amount at which the shift should occur, last 3 bits is used

FUNC. FIELD Bit (13:11)	OPERATION
101	Shift Left
110	Shift Right

# Memory Reference Instruction

## Memory Reference Type :-

LOAD, LOADI

 

### Field Description:

- Opcode** : 5 bits field:  
Bit(15:14) : **00**  
Bit (13:11) : **Functional Field**:- 3 bit field to describe the operation to be performed.
- Rd**: 3 bit field for destination register
- Data** : 8 bit field : For LOAD :- 8 bit address  
For LOADI :- 8 bit data


FUNC. FIELD Bit (13:11)	OPERATION
101	LOAD
100	LOADI

# Memory Reference Instruction

---
 
## Memory Reference Type :-

**STORE** : To store the data from register to the data memory




### Field Description:

1. **Opcode** : 5 bits(00 011)
2. **Address MSB**:3 bit field for Address Location MSB
3. **RS**: 3 bit field for source register
4. **Address LSB** : 5 bit field for Address Location LSB

# Branching Instruction
 
## Branch Type :-

JUMP (Unconditional Jump)  
JUMPZ (Conditional Jump if zero flag set in ALU)



### Field Description:

1. **Opcode** : 5 bits field:  
Bit(15:14) :01  
Bit (13:11) : **Functional Field**:- 3 bit field to describe the operation to be performed.
2. **Address** : 10 bit field for Address Location

FUNC. FIELD Bit (13:11)	OPERATION
111	JUMP
110	JUMPZ




# Miscellaneous Instruction

---

## Miscellaneous:-
 
### **RET :**


- To return from the interrupt.
- Used at the end of ISR to resume operation after interrupt



### Field Description:

1. **Opcode** : 5 bits(00 001)


### **NOP : No operation**

 

### Field Description:

1. **Opcode** : 5 bits(00 000)

# RISC-CPU

 

Port Name	Description
Clk	Clk Input
Rst	Reset Signal
Data_memory_read	8 bit output from data memory
Interrupt	External interrupt pulse
Instruction	16 bit instruction read from instruction memory
PC_Value	Current Program counter to Instruction Memory
Mem_write_data	8 bit data to Data memory
Mem_write_add	Write address to data memory
Mem_read_add	Read address to data memory
Mem_write_en	Data memory write enable signal

# RISC CPU

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RISC_CPU is
    Port ( clk : in STD_LOGIC;
          rst : in STD_LOGIC;
          interrupt : in STD_LOGIC;

          -----Instruction Memory related-----
          instruction : in STD_LOGIC_VECTOR (15 downto 0); ---from instruction memory
          Pc_value : out STD_LOGIC_VECTOR (8 downto 0); --- to instruction memory

          -----data memory related-----
          data_memory_read : in std_logic_vector(7 downto 0); ---read data from data memory
          mem_write_en : out STD_LOGIC;
          mem_read_add : out std_logic_vector(7 downto 0);
          mem_write_add : out std_logic_vector(7 downto 0);
          mem_write_data : out std_logic_vector(7 downto 0)
    );
end RISC_CPU;
```

```
architecture Behavioral of RISC_CPU is
    component Interrupt_Synchr is
        Port ( Clk : in STD_LOGIC;
              Reset : in STD_LOGIC;
              Interrupt : in STD_LOGIC;
              Int_Syn_Pulse : out STD_LOGIC
            );
    end component;
    component Controller_and_decoder is
        Port ( clk : in STD_LOGIC;
              Instruction_temp : in STD_LOGIC_VECTOR (4 downto 0);
              reset : in STD_LOGIC;
              Int_Syn_Pulse : in STD_LOGIC;
              PC_Sel_Control : out STD_LOGIC_VECTOR(1 downto 0);
              PC_Int_Save : out STD_LOGIC;
              ALU_Op_Sel : out STD_LOGIC_VECTOR (2 downto 0);
              Reg_Write_En : out STD_LOGIC;
              Memory_Write_En : out STD_LOGIC
            );
    end Component;
```

# RISC CPU

```

component data_path is
  Port ( clk : in STD_LOGIC;
         rst : in STD_LOGIC;
         Instruction:in std_logic_vector(15 downto 0);
         --from Controller-----
         reg_write_en : in STD_LOGIC;
         pc_int_save : in std_logic;
         pc_mux_sel : in STD_LOGIC_VECTOR (1 downto 0);
         alu_cntrl_sel : in STD_LOGIC_VECTOR (2 downto 0);
         --from memory-----
         data_memory_read: in std_logic_vector(7 downto 0);
         --to memory-----
         Imm_Load_Addr : out STD_LOGIC_VECTOR (7 downto 0);
         Store_Addr : out STD_LOGIC_VECTOR (7 downto 0);
         mem_write_data: out std_logic_vector(7 downto 0);
         pc : out STD_LOGIC_VECTOR (9 downto 0)
       );
end component data_path;

-- interrupt block signal
signal temp_int_syn_pulse : std_logic;
signal temp_reg_write_en : std_logic;
signal temp_pc_mux_sel : std_logic_vector(1 downto 0);
signal temp_alu_cntrl_sel :std_logic_vector(2 downto 0);
signal temp_pc_int_save : std_logic;
begin
  uut1 : Interrupt_Synchr port map ( --input signals
    clk => clk , reset => rst , interrupt => interrupt
    -- output signal
    int_syn_pulse => temp_int_syn_pulse);
end uut1;

-- input signals of controller
clk => clk, reset => rst ,
Instruction_temp => instruction (15 downto 11),
Int_Syn_Pulse => temp_int_syn_pulse,


--output signals of controller
PC_Sel_Control => temp_pc_mux_sel ,
PC_Int_Save => temp_pc_int_save,
ALU_Op_Sel => temp_alu_cntrl_sel,
Reg_Write_En => temp_reg_write_en,
Memory_Write_En => mem_write_en);

-- Controller
[ uut2 : Controller_and_decoder port map (
  rst =>rst,
  Instruction=>Instruction,
  --from Controller-----
  reg_write_en =>temp_reg_write_en,
  pc_int_save => temp_pc_int_save,
  pc_mux_sel => temp_pc_mux_sel ,
  alu_cntrl_sel => temp_alu_cntrl_sel,
  --from memory-----
  data_memory_read=>data_memory_read,
  --to memory-----
  Imm_Load_Addr =>mem_read_add,
  Store_Addr=> mem_write_add,
  mem_write_data=>mem_write_data,
  pc =>Pc_value
);
end Behavioral;

[ uut3: data_path port map ( clk => clk,
  rst =>rst,
  Instruction=>Instruction,
  --from Controller-----
  reg_write_en =>temp_reg_write_en,
  pc_int_save => temp_pc_int_save,
  pc_mux_sel => temp_pc_mux_sel ,
  alu_cntrl_sel => temp_alu_cntrl_sel,
  --from memory-----
  data_memory_read=>data_memory_read,
  --to memory-----
  Imm_Load_Addr =>mem_read_add,
  Store_Addr=> mem_write_add,
  mem_write_data=>mem_write_data,
  pc =>Pc_value
);
end Behavioral;

```

# Data Path

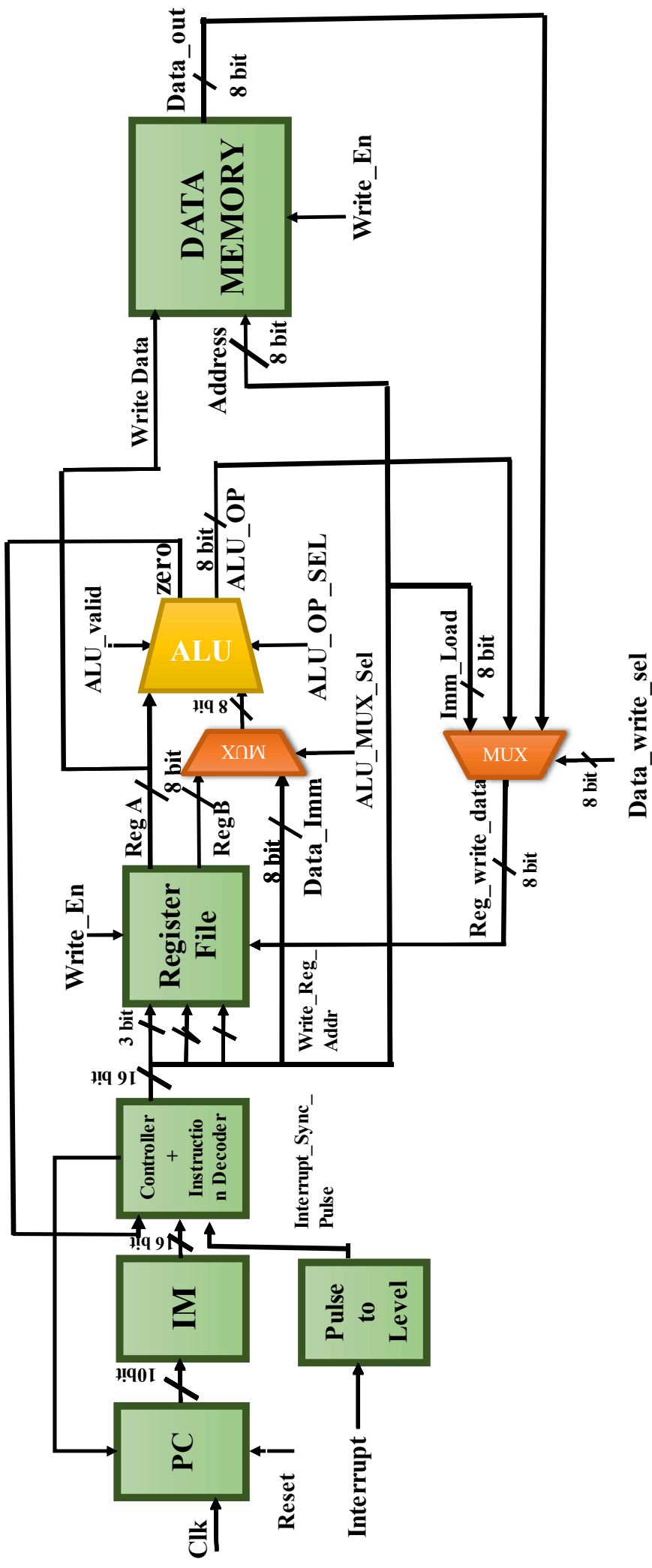

# Data Path Module

entity data\_path is

```
Port ( clk : in STD_LOGIC;
      rst : in STD_LOGIC;
      Instruction:in std_logic_vector(15 downto 0);
      --from Controller---
      reg_write_en : in STD_LOGIC;
      pc_int_save : in std_logic;
      pc_mux_sel : in STD_LOGIC_VECTOR (1 downto 0);
      alu_cntrl_sel : in STD_LOGIC_VECTOR (2 downto 0);
      --from memory-----
      data_memory_read: in std_logic_vector(7 downto 0);
      --to memory-----
      Imm_Load_Addr : out STD_LOGIC_VECTOR (7 downto 0);
      Store_Addr : out STD_LOGIC_VECTOR (7 downto 0);
      mem_write_data: out std_logic_vector(7 downto 0);
      pc : out STD_LOGIC_VECTOR (9 downto 0)
    );
end data_path;
```

architecture Behavioral of data\_path is

```
--signal declaration for Register file
signal temp_Write_Reg_Data : std_logic_vector (7 downto 0);
signal temp_RegA_Out : std_logic_vector (7 downto 0);
signal temp_RegB_Out : std_logic_vector (7 downto 0);

-- signal declaration for alu mux sel out
signal alu_mux_sel_out : std_logic_vector (7 downto 0);

--signal declaration for alu output
signal temp_alu_outdata : std_logic_vector (7 downto 0);
signal int_zero_restore: std_logic;
```

```
---Signal Declaration for Decoding-----
signal temp_RegBAddr, temp_RegBAddr,temp_write_Reg_addr : STD_LOGIC_VECTOR (2 downto 0);
signal temp_pc_jump_addr :STD_LOGIC_VECTOR (9 downto 0);
signal temp_pc_branch_sel :std_logic;
signal temp_Imm_Load_Addr,temp_data_imm: STD_LOGIC_VECTOR (7 downto 0);
signal temp_reg_write_mux_sel: STD_LOGIC_VECTOR(1 downto 0);
signal temp_ALU_Mux_Sel : std_logic;
signal temp_zero,temp_ALU_Valid : std_logic;

component Decoding is
Port ( Instruction : in STD_LOGIC_VECTOR (15 downto 0);
      Zero : in STD_LOGIC;
      RegA_Addr : out STD_LOGIC_VECTOR (2 downto 0);
      RegB_Addr : out STD_LOGIC_VECTOR (2 downto 0);
      Write_Reg_Addr : out STD_LOGIC_VECTOR (2 downto 0);
      Data_Imm : out STD_LOGIC_VECTOR (7 downto 0);
      Imm_Load_Addr : out STD_LOGIC_VECTOR (7 downto 0);
      Store_Addr : out STD_LOGIC_VECTOR (7 downto 0);
      PC_Jump_Addr : out STD_LOGIC_VECTOR (9 downto 0);
      ALU_Mux_Sel : out STD_LOGIC;
      ALU_Valid :out std_logic;
      PC_Jump_Sel : out STD_LOGIC;
      Reg_Write_Mux_Sel : out STD_LOGIC_VECTOR(1 downto 0));
end component Decoding;

component Program_Counter is
Port ( Clk : in STD_LOGIC;
      Reset : in STD_LOGIC;
      PC_Jump_Addr : in STD_LOGIC_VECTOR (9 downto 0);
      PC_Jump_Sel : in STD_LOGIC;
      PC_Int_save : in Std_logic;
      PC_Sel_Control : in STD_LOGIC_VECTOR (1 downto 0);
      PC : out STD_LOGIC_VECTOR (9 downto 0));
end component;
```



# Data Path Module

```

component Register_File is
Port ( Clk : in STD_LOGIC;

      Write_Reg_Data : in STD_LOGIC_VECTOR (7 downto 0);
      RegA_Addr : in STD_LOGIC_VECTOR (2 downto 0);
      RegB_Addr : in STD_LOGIC_VECTOR (2 downto 0);
      Write_Reg_Addr : in STD_LOGIC_VECTOR (2 downto 0);
      Write_En : in STD_LOGIC;
      RegA_Out : out STD_LOGIC_VECTOR (7 downto 0);
      RegB_Out : out STD_LOGIC_VECTOR (7 downto 0));
end component;

component ALU_MUX is
Port ( ALU_MUX_SEL : in STD_LOGIC;

      RegB_Out : in STD_LOGIC_VECTOR (7 downto 0); -- Register File 2nd input
      Data_Imm : in STD_LOGIC_VECTOR (7 downto 0); -- Immediate data extracted from the instruction
      Reg_B : out STD_LOGIC_VECTOR (7 downto 0)); -- 2nd input of ALU
end component;

component ALU_unit is
Port ( Clk, Reset : in std_logic;
      ALU_Valid : in std_logic;
      Int_Save, Int_Restore : in std_logic;
      data_in1 : in STD_LOGIC_VECTOR (7 downto 0);
      data_in2 : in STD_LOGIC_VECTOR (7 downto 0);
      data_output : out STD_LOGIC_VECTOR (7 downto 0);
      zero_flag : out STD_LOGIC;
      alu_op_sel : in STD_LOGIC_VECTOR (2 downto 0));
end component;

component reg_write_mux is
Port ( ALU_out : in STD_LOGIC_VECTOR (7 downto 0);
      memory_out : in STD_LOGIC_VECTOR (7 downto 0);
      imm_load : in STD_LOGIC_VECTOR (7 downto 0);
      reg_write_mux : in STD_LOGIC_VECTOR (4 downto 0);
      write_reg_data : out STD_LOGIC_VECTOR (7 downto 0));
end component;

```

```

begin
|dut1 : Program_Counter_port_map ( Clk => clk ,
Reset => rst ,
PC_Jump_Addr => temp_pc_jump_addr ,
PC_Jump_Sel => temp_pc_branch_sel ,
PC_Int_Save => pc_int_save ,
PC_Sel_Control => pc_mux_sel ,
PC => pc);

|dut2 : Register_File_port_map ( Clk => clk ,
Write_Reg_Data => temp_Write_Reg_Data ,
RegA_Addr => temp_RegAaddr ,
RegB_Addr => temp_RegBaddr ,
Write_Reg_Addr => temp_write_Reg_addr ,
Write_En => reg_write_en ,
RegA_Out => temp_RegA_Out ,
RegB_Out => temp_RegB_Out);

|dut3 : ALU_MUX_port_map ( ALU_MUX_SEL => temp_alu_mux_sel ,
RegB_Out => temp_RegB_Out ,
Data_Imm => temp_data_imm ,
Reg_B => alu_mux_sel_out);

|dut4 : ALU_unit_port_map( Clk => clk ,
Reset => rst ,
ALU_Valid=>temp_ALU_Valid ,
Int_Save => pc_int_save ,
Int_Restore => Int_zero_restore ,
data_in1 => temp_RegA_Out ,
data_in2 => alu_mux_sel_out ,
alu_op_sel => alu_cntrl_sel ,
zero_flag => temp_zero ,
data_output => temp_alu_outdata);

```

# Data Path Module

```

dut5 : reg_write_mux port map ( ALU_out => temp_alu_outdata ,
                                memory_out => data_memory_read ,
                                imm_load => temp_imm_load_addr ,
                                reg_write_mux => temp_reg_write_mux_sel ,
                                write_reg_data => temp_write_reg_data ) ;

dut6: Decoding port map(
    Instruction => Instruction,
    Zero => temp_Zero,
    RegA_Addr => temp_RegAAddr,
    RegB_Addr => temp_RegBAddr,
    Write_Reg_Addr -> temp_Write_Reg_Addr,
    Data_Imm -> temp_Data_Imm,
    Imm_Load_Addr -> temp_Imm_Load_Addr,
    Store_Addr -> Store_Addr,
    PC_Jump_Addr => temp_PC_Jump_Addr,
    ALU_Mux_Sel => temp_ALU_Mux_Sel,
    ALU_Valid => temp_ALU_Valid,
    PC_Jump_Sel => temp_pc_branch_sel,
    Reg_Write_Mux_Sel => temp_Reg_Write_Mux_Sel
);


mem_write_data<temp_RegA_Out;
Int_zero_restore<pc_mux_sel(1) and pc_mux_sel(0);
Imm_Load_Addr <temp_Imm_Load_Addr;

--end Behavioral;
```



# Functional Units

## ALU Design :

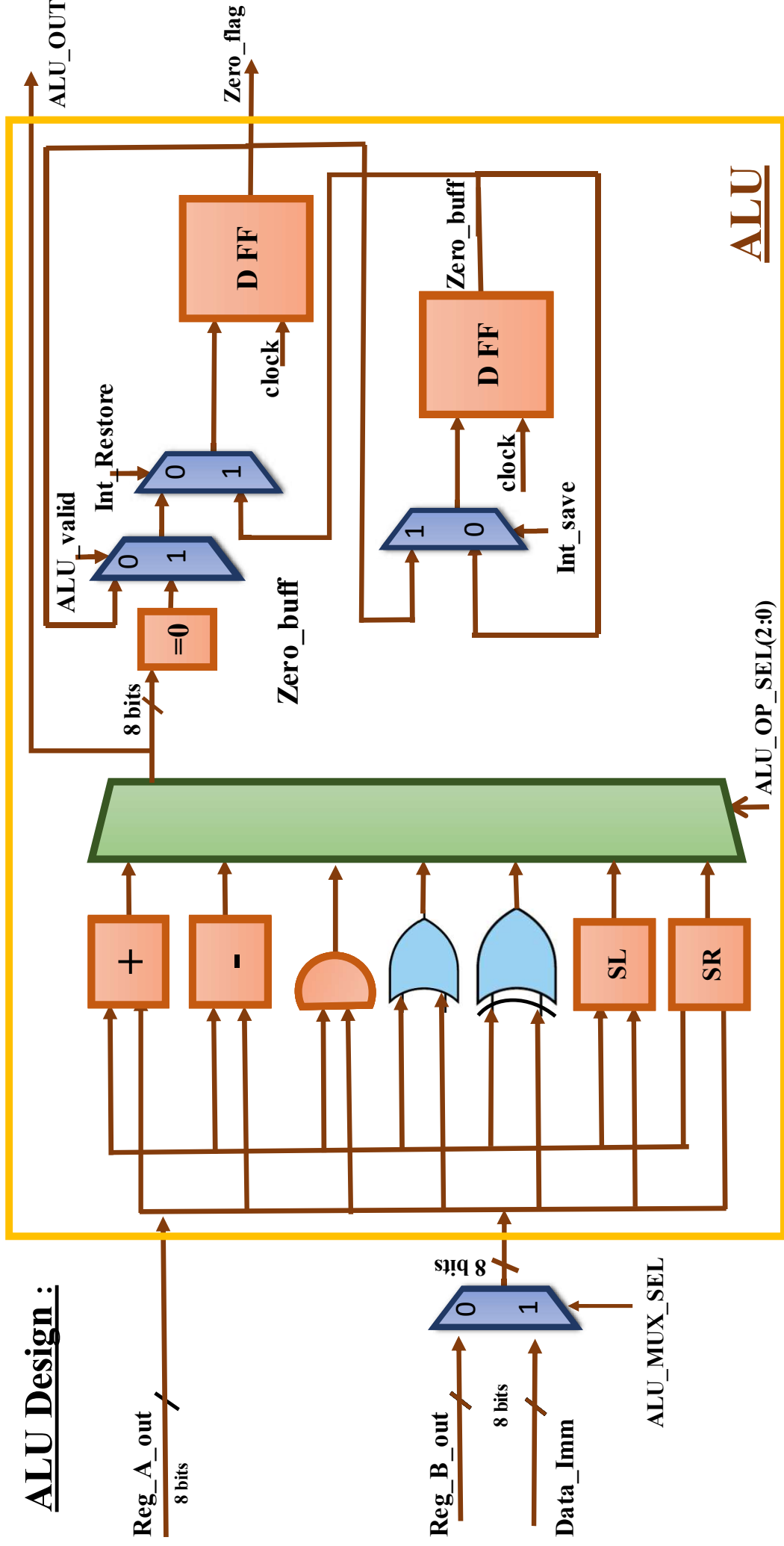

# ALU Design Code

```

entity ALU_unit is
generic(size : integer := 8;
        no_bit : integer := 3);
Port ( Clk, Reset : in std_logic;
      ALU_Valid : in std_logic;
      Int_Save, Int_Restore : in std_logic;
      data_in1 : in STD_LOGIC_VECTOR (size-1 downto 0);
      data_in2 : in STD_LOGIC_VECTOR (size-1 downto 0);
      data_output : out STD_LOGIC_VECTOR (size-1 downto 0);
      zero_flag : out STD_LOGIC;
      alu_op_sel : in STD_LOGIC_VECTOR (no_bit-1 downto 0));
end ALU_unit;

```

architecture Behavioral of ALU\_unit is

```

signal zero_f3, zero_f2, zero_f1, zero_temp, zero_buff: std_logic;
signal data_out : std_logic_vector (size-1 downto 0);
begin

```

```

zero_f1 <= '1' when (data_out="00") else '0';
zero_f2<=zero_f1 when ALU_Valid='1' else zero_temp;
zero_f3<=zero_buff when Int_Restore='1' else zero_f2;

```

```

process(clk)
begin
    if (clk'event and clk='1') then
        if (Reset='1') then
            zero_temp<='0';
        else
            zero_temp<=zero_f3;
        end if;
    end if;
end process;

```

```

process(clk)
begin
    if (clk'event and clk='1') then
        if (Reset='1') then
            zero_buff<='0';
        else
            if (Int_Save='1') then
                zero_buff<=zero_temp;
            end if;
        end if;
    end if;
end process;

zero_flag<=zero_temp;
data_output <= data_out;
process(data_in1 , data_in2 , alu_op_sel)
begin
    case alu_op_sel is
        when "000" =>
            data_out <= data_in1 + data_in2 ;
        when "001" =>
            data_out <= data_in1 + (not(data_in2) + 1);
        when "010" =>
            data_out <= data_in1 xor data_in2 ;
        when "011" =>
            data_out <= data_in1 or data_in2;
        when "100" =>
            data_out <= data_in1 and data_in2;
    end case;
end process;

```

# ALU Design Code

```
when "101" =>
  case data_in2(2 downto 0) is
    when "000" =>
      data_out <= data_in1(7 downto 0);
    when "001" =>
      data_out <= data_in1(6 downto 0) & '0';
    when "010" =>
      data_out <= data_in1(5 downto 0) & "00";
    when "011" =>
      data_out <= data_in1(5 downto 0) & "00";
    when "100" =>
      data_out <= data_in1(4 downto 0) & "000";
    when "101" =>
      data_out <= data_in1(3 downto 0) & "0000";
    when "110" =>
      data_out <= data_in1(2 downto 0) & "00000";
    when "111" =>
      data_out <= data_in1(1 downto 0) & "0000000";
    when others =>
      data_out <= data_in1(0) & "00000000";
  end case;
end process;
```

```
when "110" =>
  case data_in2(2 downto 0) is
    when "000" =>
      data_out <= data_in1(7 downto 0);
    when "001" =>
      data_out <= '0' & data_in1(7 downto 1);
    when "010" =>
      data_out <= "00" & data_in1(7 downto 2);
    when "011" =>
      data_out <= "000" & data_in1(7 downto 3);
    when "100" =>
      data_out <= "0000" & data_in1(7 downto 4);
    when "101" =>
      data_out <= "00000" & data_in1(7 downto 5);
    when "110" =>
      data_out <= "000000" & data_in1(7 downto 6);
    when "111" =>
      data_out <= "0000000" & data_in1(7);
    when others =>
      data_out <= (others => '0');
  end case;
when others =>
  data_out <= (others => '0');
end case;
end process;
--end Behavioral;
```

# ALU MUX Design Code

---

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


entity ALU_MUX is
    Port ( ALU_MUX_SEL : in STD_LOGIC;
          RegB_Out : in STD_LOGIC_VECTOR (7 downto 0); -- Register File 2nd input
          Data_Imm : in STD_LOGIC_VECTOR (7 downto 0); --Immediate data extracted from the instruction
          Reg_B : out STD_LOGIC_VECTOR (7 downto 0)); --2nd input of ALU
    -end ALU_MUX;

Architecture Behavioral of ALU_MUX is
    --ALU_MUX_SEL : Control signal from controller
    --RegB_Out : Register File 2nd input
    --Data_Imm : Immediate data extracted from the instruction
    --Reg_B : 2nd input of ALU
    begin
        Reg_B <= Data_Imm when ALU_MUX_SEL = '1' else
            RegB_Out;
    -end Behavioral;
```

# Functional Units

---

## Register File :

 

- Eight 8 bit Registers.
- Read is always Transparent
- Write only on clock edge controlled by the Write\_Enable signal

# Register File Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Register_File is
    port ( Clk : in STD_LOGIC;
           Write_Reg_Data : in STD_LOGIC_VECTOR (7 downto 0);
           RegA_Addr : in STD_LOGIC_VECTOR (2 downto 0);
           RegB_Addr : in STD_LOGIC_VECTOR (2 downto 0);
           Write_Reg_Addr : in STD_LOGIC_VECTOR (2 downto 0);
           Write_En : in STD_LOGIC;
           RegA_Out : out STD_LOGIC_VECTOR (7 downto 0);
           RegB_Out : out STD_LOGIC_VECTOR (7 downto 0));
end Register_File;

--Clk input
--data to write
--RegA address to read
--RegB address to read
--Write register address
--Register Write enable
--Register A data
--Register B data

architecture Behavioral of Register_File is

    type ramtype is array (7 downto 0) of std_logic_vector(7 downto 0);
    signal mem1 : ramtype;


begin
    --Write to all register
    process(clk)
    begin
        if (clk'event and clk='1') then
            --if (Reset='0') then No reset value...Registers can be initiated using Load and LoadI instructions
            -- mem1<=(others=>'0'); ---initialized to 0
            if (Write_En = '1') then
                mem1(to_integer(unsigned(Write_Reg_Addr)))<=Write_Reg_Data;
            end if;
        end if;
    end process;

    ---Read Register-----
    RegA_Out<= mem1(to_integer(unsigned(RegA_Addr)));
    RegB_Out<= mem1(to_integer(unsigned(RegB_Addr)));
end Behavioral;
```

# Functional Units

---

## Register Write Mux :

 

- Register Write Mux is used to select the data to be written to Register file. ALU\_Out (R Type Instruction) or Memory out from data memory (Load Instruction) or Immediate data from instruction (LoadI instruction) is selected based on the instruction being executed. Reg\_Write\_Mux\_Sel is generated from controller decoder module.



# Register Write Mux

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;


entity reg_write_mux is
    Port ( ALU_out : in STD_LOGIC_VECTOR (7 downto 0);
          memory_out : in STD_LOGIC_VECTOR (7 downto 0);
          imm_load : in STD_LOGIC_VECTOR (7 downto 0);
          reg_write_mux : in STD_LOGIC_VECTOR (1 downto 0);
          write_reg_data :out STD_LOGIC_VECTOR (7 downto 0));
end reg_write_mux;

architecture Behavioral of reg_write_mux is
    --Data in registers from 3 different sources
    --ALU_out : Data in register come from ALU
    --memory_out : Data in registers come from Data Memory
    --imm_load : Data in registers come immediately
    --reg_write_mux : Select from which source data come in the register
    --write_reg_data : write the data in the registers
begin
    write_reg_data<= ALU_out when reg_write_mux ="00" else
        memory_out when reg_write_mux ="01" else
        imm_load when reg_write_mux ="10" else
        ALU_out;
end Behavioral;
```



# Functional Units

## Program Counter :-

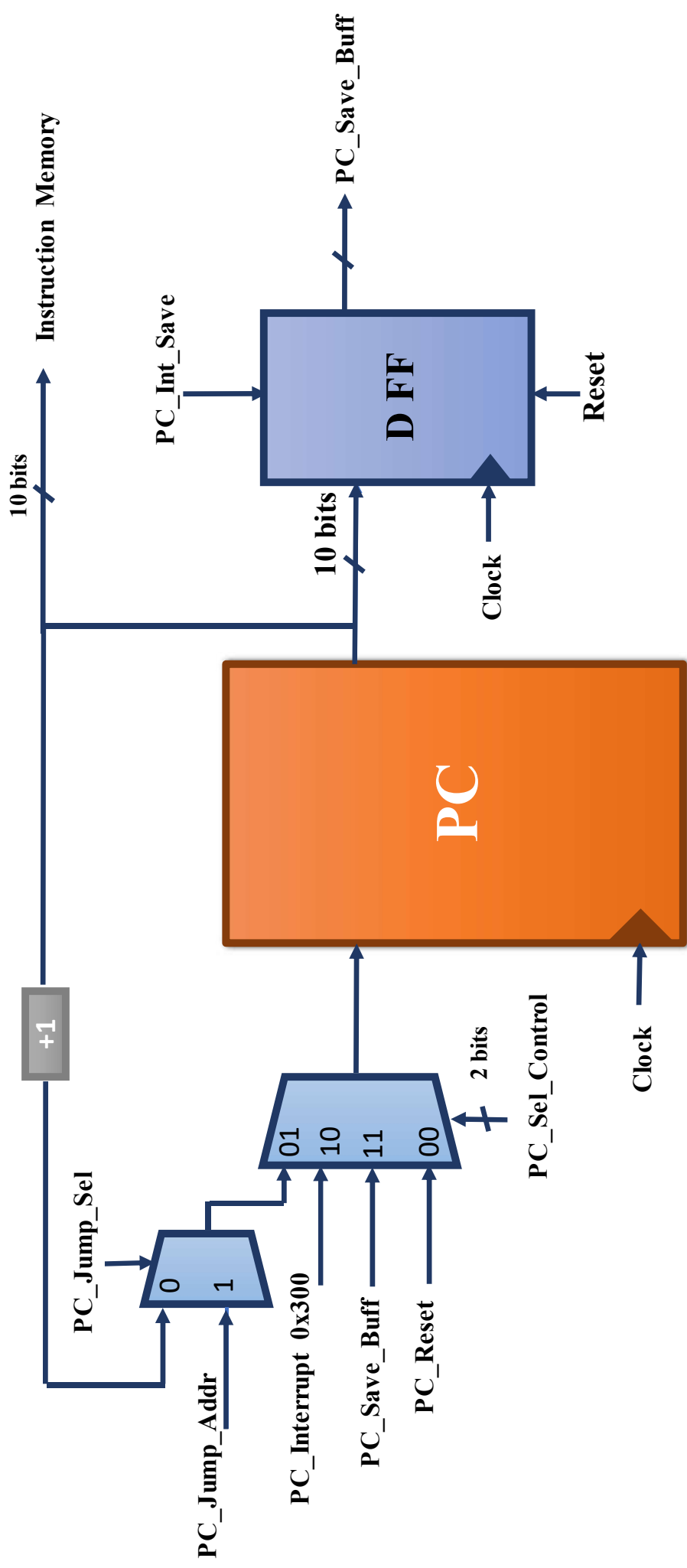

# Program Counter Code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Program_Counter is
    Port ( Clk : in STD_LOGIC;
          Reset : in STD_LOGIC;
          PC_Jump_Addr : in STD_LOGIC_VECTOR (9 downto 0);
          PC_Jump_Sel : in STD_LOGIC;
          PC_Int_Save : in Std_logic;
          PC_Sel_Control : in STD_LOGIC_VECTOR (1 downto 0);
          PC : out STD_LOGIC_VECTOR (9 downto 0));
end Program_Counter;

architecture Behavioral of Program_Counter is
    signal Pc_Temp, Pc_Temp1, Pc_Temp2, pc_save_buff: std_logic_vector(9 downto 0);

begin
    Pc_Temp <= Pc_Jump_Addr when PC_Jump_Sel = '1' else
        Pc_Temp2+1;

    Pc_Temp1 <= b"00000000000" when PC_Sel_Control="00" else -----Reset PC_Value
        Pc_Temp when PC_Sel_Control="01" else -----Normal operation
        b"11000000000" when PC_Sel_Control="10" else ---Interrupt State
        pc_save_buff;
        ---Restoring saved PC state

    -----Program Counter part
    process (clk, Reset)
    begin
        if (clk'event and clk='1') then
            if (Reset='1') then
                PC_Temp2<=(others =>'0');
            else
                PC_Temp2<=PC_Temp1;
            end if;
        end if;
    end process;
    PC<=PC_Temp2;
    -----Saving the PC value to intermediate signal-----
    process (clk)
    begin
        if (Clk'event and Clk='1') then
            if (Reset='1') then
                pc_save_buff<=(Others=>'0');
            else
                if (PC_int_save='1') then
                    pc_save_buff<=PC_Temp2;
                end if;
            end if;
        end if;
    end process;

    end Behavioral;
end

```

# Interrupt Pulse Detector Code

```
entity Interrupt_Synchr is
    Port ( Clk : in STD_LOGIC;
           Reset : in STD_LOGIC;
           Interrupt : in STD_LOGIC;
           Int_Syn_Pulse : out STD_LOGIC);
end Interrupt_Synchr;

Architecture Behavioral of Interrupt_Synchr is
    Signal I,I1, I2, I3 : std_logic;

begin
    --Pulse to level signal----
    process(Interrupt, Reset)
    begin
        if(Reset='1') then
            I<='0';
        elsif(Interrupt'event and Interrupt='1') then
            I<= not I;
        end if;
    end process;


    ---Synchronizer
    process(clk,Reset)
    begin
        if(Reset='1') then
            I1<='0';
            I2<='0';
            I3<='0';
        elsif(clk'event and clk='1') then
            I1<=I;
            I2<=I1;
            I3<=I2;
        end if;
    end process;

    Int_Syn_Pulse<=I2 xor I3;
end Behavioral;
```

# Functional Units

## Controller + Instruction

### Decoder :

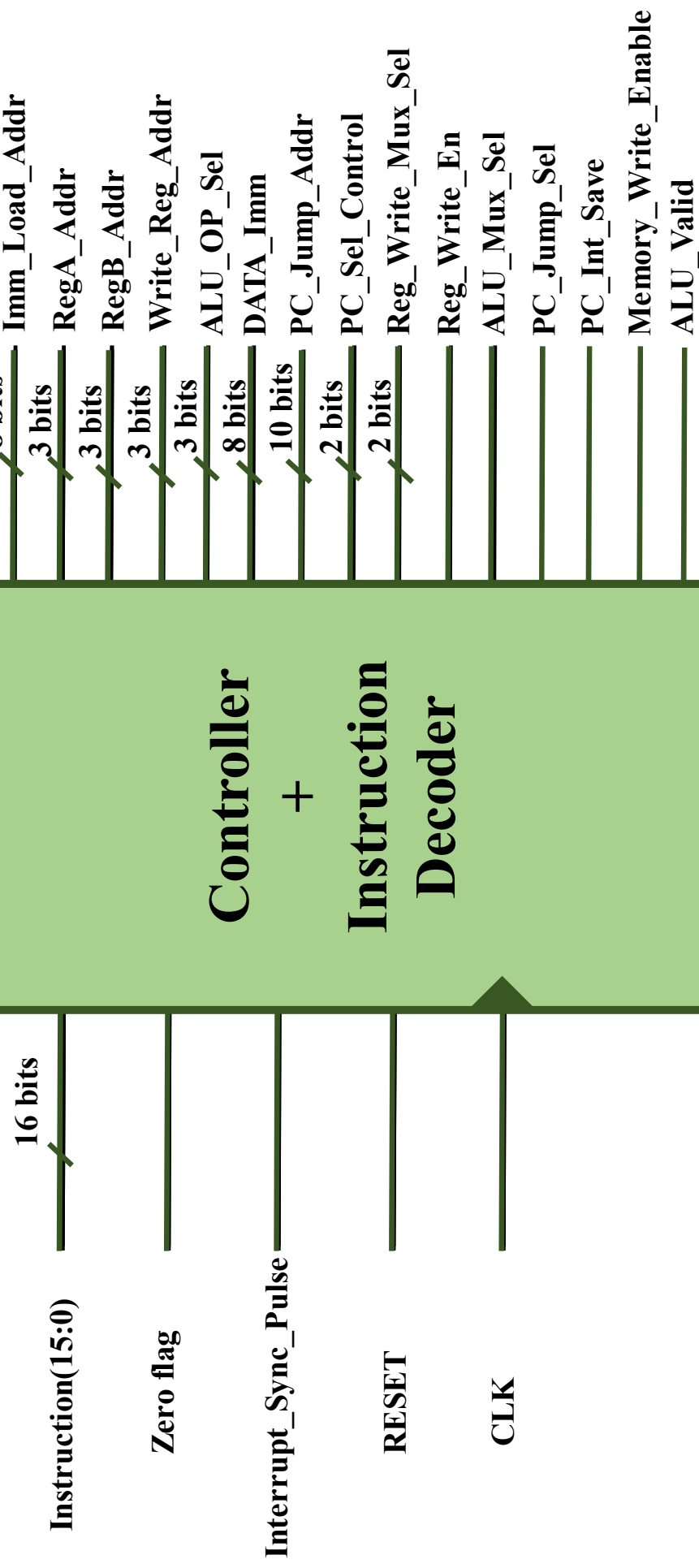

# Control Signals

## 1-bit Control Signal :

Signal \ Value	0	1
<b>Reg_Write_En</b>	No Operation	Write data written to destination register in clock edge
<b>ALU_Mux_Sel</b>	2 <sup>nd</sup> Input of ALU from Reg B	2 <sup>nd</sup> Input of ALU from immediate data in instruction
<b>PC_Jump_Sel</b>	PC=PC+1	PC=Jump Address
<b>ALU_Valid</b>	Not a valid ALU operation, Zero flag wont get updated	Indicate Valid ALU operation
<b>PC_Int_Save</b>	PC_Save buffer retains the old value	PC_Save_Buff updates with current PC value
<b>Memory_Write_Enable</b>	No Operation	For Store instruction(When user wants to write in the data memory)

# Control Signals

## 2-bits Control Signal :

Signal \ Value	00	01	10	11
<b>PC_Sel_Control</b>	Reset Mode	Normal Operation Mode	When Interrupt Comes, PC updates with 0x300	Returning from the Interrupt PC updates with saved PC value from buffer
<b>Reg_Write_Mux_Sel</b>	write_reg_data<= ALU_Out (R Instruction)	write_reg_data<= Memory_Out (Load operation)	write_reg_data<= Imm_Load (LoadI operation)	write_reg_data<= ALU_Out

# Control Signals

## 3-bits Control Signal :

Signal	Value	
<b>RegA_Addr</b>	Source Register 1 Address to Register File	Instruction(7:5)
<b>RegB_Addr</b>	Source Register 2 Address to Register File	Instruction(4:2)
<b>Write_Reg_Addr</b>	Destination Register Address to Register File	Instruction(4:2)
<b>ALU_OP_Sel</b>	000: Add Immediate and Add Instruction 001: Subtract Instruction 010: Xor Instruction 011: Or Instruction 100: AND Instruction 101: Shift Left 110: Shift Right 111: No operation	“111” during Interrupt_Save & restore state “000” if ADDI instruction Else Instruction(13:11)

# Control Signals

## 8-bits Control Signal :

Signal \ Value		
Store_Addr	Write Address to Data memory during store instruction	Instruction(10:8)&Instruction(4:0)
Imm_Load_Add	Immediate Data for LOADI instruction Data Memory Read Address for LOAD Instruction	Instruction(7:0)
DATA_Imm	Immediate Data for ADDI Instruction, input to the ALU Mux	Instruction(13:11)&Instruction(4:0)



# Control Signals

---

## 10-bits Control Signal :

Value Signal			
PC_Jump_Addr	Address to branch during a JUMP or JUMPZ	Instruction(9:0)	

# Decoder Code

```

end entity Decoding is
]
Port ( Instruction : in STD_LOGIC_VECTOR (15 downto 0);
      Zero : in STD_LOGIC;
      RegA_Addr : out STD_LOGIC_VECTOR (2 downto 0);
      RegB_Addr : out STD_LOGIC_VECTOR (2 downto 0);
      Write_Reg_Addr : out STD_LOGIC_VECTOR (2 downto 0);
      Data_Imm : out STD_LOGIC_VECTOR (7 downto 0);
      Imm_Load_Addr : out STD_LOGIC_VECTOR (7 downto 0);
      Store_Addr : out STD_LOGIC_VECTOR (7 downto 0);
      PC_Jump_Addr : out STD_LOGIC_VECTOR (9 downto 0);
      ALU_Mux_Sel : out STD_LOGIC;
      ALU_Valid : out STD_LOGIC;
      PC_Jump_Sel : out STD_LOGIC;
      Reg_Write_Mux_Sel : out STD_LOGIC_VECTOR (1 downto 0));
end Decoding;

]architecture Behavioral of Decoding is
]begin

      RegA_Addr <= Instruction(7 downto 5);
      RegB_Addr <= Instruction(4 downto 2);
      Write_Reg_Addr <= Instruction(10 downto 8);
      Data_Imm <= Instruction(13 downto 11) & Instruction(4 downto 0);
      Imm_Load_Addr <= Instruction(7 downto 0);
      Store_Addr <= Instruction(10 downto 8) & Instruction(4 downto 0);
      PC_Jump_Addr <= Instruction(9 downto 0);
      ALU_Mux_Sel <= Instruction(14);
      PC_Jump_Sel <= '1' when Zero='1' and Instruction(15 downto 11)="00111" else
        '1' when Instruction(15 downto 11)="00110" else
        '0';

      Reg_Write_Mux_Sel <= "01" when Instruction(15 downto 11)="00101" else
        "10" when Instruction(15 downto 11)="00100" else
        "00";

      ALU_Valid <= Instruction(14) or Instruction(15);

end Behavioral;


-- Source Register1
-- Source Register2
-- Destination Register
-- Immediate Data for ADDI and for shiftright and shiftright only(Instruction(4 downto 0)
-- Immediate Data Memory Address for LOAD and Immediate Data for LOADI
-- Destination Memory Address for STORE
-- PC Jump Address for JUMP and JUMPZ Instruction
-- Selection of second input of ALU(1:Immediate Data ,0:Register Data)
-- PC_Jump_Sel=> 1:for Jump and Successful JUMPZ , 0:PC won't jump(normal operation)

-- When there is need to write in registers(LOAD:01 and LOADI:10 Instruction)

--indicating a valid ALU operation is going on

```

# State Diagram

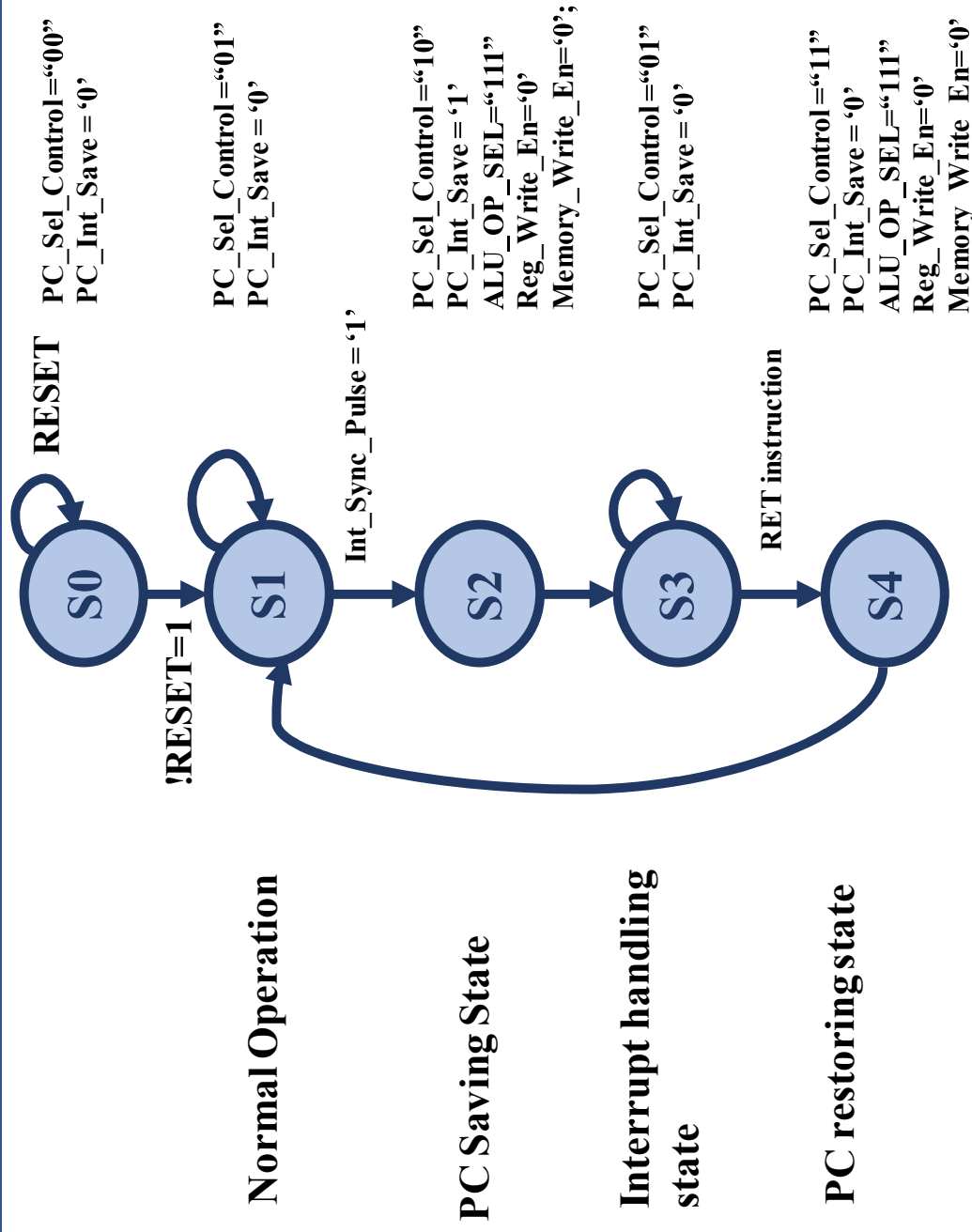

# Description

State	Description	Relevant Control Signals
S0	Reset state, where all the control signals will be zero and it will wait here till reset is removed	PC_Sel_Control = “00” PC_Int_Save = ‘0’
S1	This is the normal operation state, where PC will be incremented or branched depending on the instruction. State will wait for interrupt to happen	PC_Sel_Control = “01” PC_Int_Save = ‘0’
S2	If interrupt occurs, processor comes to this state for context saving of PC and zero flag to buffers	PC_Sel_Control = “10” PC_Int_Save = ‘1’
S3	Interrupt service routine (ISR) getting handled and waits for return instruction	PC_Sel_Control = “01” PC_Int_Save = ‘0’
S4	PC and Zero flag get restored in this state. Returning from interrupt to main thread	PC_Sel_Control = “11” PC_Int_Save = ‘0’

# Controller And Decoder Code

```

entity Controller_and_decoder is
Port ( clk : in STD_LOGIC;
      Instruction_temp : in STD_LOGIC_VECTOR (4 downto 0);
      reset : in STD_LOGIC;
      Int_Syn_Pulse : in STD_LOGIC;
      -----Output Signals-----
      PC_Sel_Control : out STD_LOGIC_VECTOR(1 downto 0);
      PC_Int_Save : out STD_LOGIC;
      ALU_Op_Sel : out STD_LOGIC_VECTOR (2 downto 0);
      Reg_Write_En : out STD_LOGIC;
      Memory_Write_En : out STD_LOGIC);
end Controller_and_decoder;

architecture Behavioral of Controller_and_decoder is

type state is (s0,s1,s2,s3,s4);
signal pr_state,next_state : state;

begin
FSM_Block:process(clk)
begin
if(clk'event and clk='1')then
--State Registers
if(reset='1') then
pr_state<=s0;
else
pr_state<=next_state;
end if;
end if;
end process;

FSM_Combinational_Block: process(reset,pr_state,Int_Syn_Pulse,Instruction_temp)
begin
case pr_state is
---State 0
when s0 =>
PC_Sel_Control <= "00";
PC_Int_Save <='0';

```

# Controller And Decoder Code


```
when others=>
    PC_Sel_Control <= "00";
    PC_Int_Save <= '0';
    next_state<=s0;
end case;
end process;

ALU_Op_Sel <= "111" when pr_state=s2 or pr_state=s4 else
    "000" when Instruction_temp(4)='1' and
    Instruction_temp(3)='1' else
    Instruction_temp(2 downto 0);

Reg_Write_En <= '0' when pr_state=s2 or pr_state=s4 else
    '1' when Instruction_temp(4)='1' or
    Instruction_temp(3)='1' or
    Instruction_temp(2 downto 0)="101" or
    Instruction_temp(2 downto 0)="100" else
    '0';

Memory_Write_En <= '0' when pr_state=s2 or pr_state=s4 else
    '1' when Instruction_temp(4 downto 0)="00011" else
    '0';
end Behavioral;
```

# Testing of RISC CPU

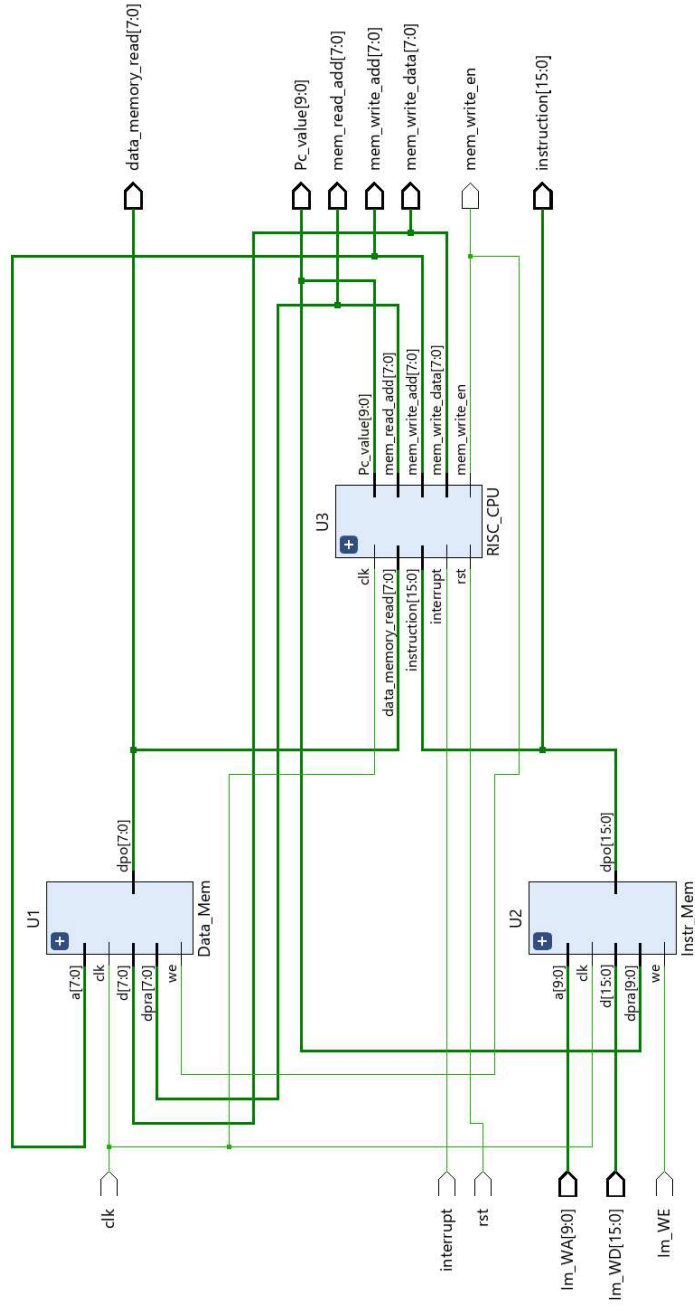

- To test RISC CPU module, Data Memory (256x8) and Instruction memory(1024x16) was instantiated using distributed simple dual port RAM.
- Instruction Memory is initialized from testbench using program stored in the text file and once initialized reset signal to the RISC CPU is de asserted.



# Top Module

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RISC_Main is
Port (
    clk : in STD_LOGIC;
    rst : in STD_LOGIC;
    interrupt : in STD_LOGIC;
    -----Instruction Memory related-----
    instruction : out STD_LOGIC_VECTOR (15 downto 0); ---from instruction memory
    Pc_value : out STD_LOGIC_VECTOR (9 downto 0); --- to instruction memory
    Im_WA : in STD_LOGIC_VECTOR (9 downto 0);
    Im_WE : in STD_LOGIC;
    Im_WD : in STD_LOGIC_VECTOR (15 downto 0);
    -----data memory related-----
    data_memory_read : out std_logic_vector(7 downto 0); ---read data from data memory
    mem_write_en : out STD_LOGIC;
    mem_read_add : out std_logic_vector(7 downto 0);
    mem_write_add : out std_logic_vector(7 downto 0);
    mem_write_data : out std_logic_vector(7 downto 0);
    );
    -----ALU Output (just for debugging)-----
    -- ALU Output : out std_logic_vector(7 downto 0)
);
end RISC_Main;

architecture Behavioral of RISC_Main is
    signal temp_data_memory_read,temp_mem_read_add,temp_mem_write_add:std_logic_vector(7 downto 0);
    signal temp_mem_write_data,temp_ALU_Output:std_logic_vector(7 downto 0);
    signal temp_instruction:STD_LOGIC_VECTOR (15 downto 0);
    signal temp_pc_value :STD_LOGIC_VECTOR (9 downto 0);
    signal temp_mem_write_en:std_logic;

```

```

component Risc_CPU is
Port ( clk : in STD_LOGIC;
    rst : in STD_LOGIC;
    interrupt : in STD_LOGIC;
    -----Instruction Memory related-----
    instruction : in STD_LOGIC_VECTOR (15 downto 0); ---from instruction memory
    Pc_value : out STD_LOGIC_VECTOR (9 downto 0); --- to instruction memory
    -----data memory related-----
    data_memory_read : in std_logic_vector(7 downto 0); ---read data from data memory
    mem_write_en : out STD_LOGIC;
    mem_read_add : out std_logic_vector(7 downto 0);
    mem_write_add : out std_logic_vector(7 downto 0);
    mem_write_data : out std_logic_vector(7 downto 0);
    );
    -----component Risc_CPU;
component Instr_Mem
Port (
    a : in STD_LOGIC_VECTOR(9 DOWNTO 0);
    d : in STD_LOGIC_VECTOR(15 DOWNTO 0);
    dpra : in STD_LOGIC_VECTOR(9 DOWNTO 0);
    clk : in STD_LOGIC;
    we : in STD_LOGIC;
    dpo : out STD_LOGIC_VECTOR(15 DOWNTO 0)
);
--END COMPONENT;
component Data_Mem
Port (
    a : in STD_LOGIC_VECTOR(7 DOWNTO 0);
    d : in STD_LOGIC_VECTOR(7 DOWNTO 0);
    dpra : in STD_LOGIC_VECTOR(7 DOWNTO 0);
    clk : in STD_LOGIC;
    we : in STD_LOGIC;
    dpo : out STD_LOGIC_VECTOR(7 DOWNTO 0)
);
--END COMPONENT;

```



# Top Module

```

U1: Data_Mem
] PORT MAP (
    a => temp_mem_write_add,
    d => temp_mem_write_data,
    dpra => temp_mem_read_add,
    clk => clk,
    we => Temp_mem_write_en,
    dpo => temp_data_memory_read
);

U2: Instr_Mem
] PORT MAP (
    a => IM_WA,
    d => IM_WD,
    dpra => temp_pc_value,
    clk => clk,
    we => IM_WE,
    dpo => temp_instruction
);

U3: Risc_CPU PORT MAP
(
    clk => clk,
    rst => rst,
    interrupt => interrupt,

    -----Instruction Memory related-----
    instruction => temp_instruction,
    Pc_value    => temp_pc_value,

    -----data memory related-----
    data_memory_read => temp_data_memory_read,
    mem_write_en    => Temp_mem_write_en,
    mem_read_add    => temp_mem_read_add,
    mem_write_add   => temp_mem_write_add,
    mem_write_data  => temp_mem_write_data
);

```

```

--ALU Output<=temp_ALU_Output;
data_memory_read <= temp_data_memory_read;
mem_write_en     <= Temp_mem_write_en;
mem_read_add     <= temp_mem_read_add;
mem_write_add    <= temp_mem_write_add;
mem_write_data   <= temp_mem_write_data;
instruction <= temp_instruction;
Pc_value        <= temp_pc_value;

--end Behavioral;

```

# Testing Code

---

Sum of first 15 Natural Numbers:-

## Main Code

```
0x0000: NOP
0x0001: LOADI R0,00H
0x0002: LOADI R1,00H
0x0003: LOADI R2,15H
0x0004: LOADI R3,01H
(L00P)
0x0005: ADDI R0,01H
0x0006: ADD R1,R0,R1
0x0007: SUB R2,R2,R3
0x0008: JUMPZ FINISH
0x0009: JUMP LOOP
(FINISH)
0x000A: STORE R1,00H
0x000B: NOP
0x000C: LOAD R5,00H
0x000D: LOAD R7,03H
0x000E: NOP
0x000F: NOP
0x0010: JUMP #0EH
```

## Interrupt

```
0x0300 : NOP
0x0301 : LOADI R5, AA
0x0302 : LOADI R6, F0
0x0303 : OR R7, R5, R6
0x0304 : STORE R7, #03
0x0305 : RET
```

**OR, AA and F0 and store in data memory location 03**

# Testbench

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use std.textio.all;
use ieee.std_logic_textio.all;
use IEEE.std_logic_unsigned.ALL;
use IEEE.NUMERIC_STD.ALL;

entity RISC_TB is
-- Port ( );
end RISC_TB;

architecture Behavioral of RISC_TB is

component RISC_Main is
Port (
clk : in STD_LOGIC;
rst : in STD_LOGIC;
interrupt : in STD_LOGIC;
-----Instruction Memory related-----
instruction : out STD_LOGIC_VECTOR (15 downto 0); ---from instruction memory
Pc_value : out STD_LOGIC_VECTOR (5 downto 0); --- to instruction memory
Im_WA : in STD_LOGIC_VECTOR (9 downto 0);
Im_WE : in STD_LOGIC;
Im_WD : in STD_LOGIC_VECTOR (15 downto 0);
-----data memory related-----
data_memory_read : out std_logic_vector(7 downto 0); ---read data from data memory
mem_write_en : out STD_LOGIC;
mem_read_add : out std_logic_vector(7 downto 0);
mem_write_add : out std_logic_vector(7 downto 0);
mem_write_data : out std_logic_vector(7 downto 0);
-----ALU Output (just for debugging)-----
-- ALU_Output : out std_logic_vector(7 downto 0)
);
end component RISC_Main;

signal rst : STD_LOGIC:= '1';
signal mem_write_en: std_logic;
signal instruction:STD_LOGIC_VECTOR (15 downto 0);
signal Pc_value: STD_LOGIC_VECTOR (9 downto 0);
signal data_memory_read,mem_read_add,mem_write_add,mem_write_data:std_logic_vector(7 downto 0);
signal Im_WA:STD_LOGIC_VECTOR (9 downto 0):="00000000000";
signal Im_WD:STD_LOGIC_VECTOR (15 downto 0):="x"0000";

constant period:time := 20 ns;
constant setup: time := 4 ns;

begin

DUT: RISC_Main port map
(
clk=>clk,
rst =>rst,
interrupt=>interrupt,
-----Instruction Memory related-----
instruction=>instruction,
Pc_value=>Pc_value,
Im_WA=>Im_WA,
Im_WE=> Im_WE,
Im_WD=>Im_WD,
-----data memory related-----
data_memory_read->data_memory_read,
mem_write_en =>mem_write_en,
mem_read_add =>mem_read_add,
mem_write_add=>mem_write_add,
mem_write_data =>mem_write_data
-----ALU Output (just for debugging)-----
-- ALU_Output =>ALU_Output
);

```

# Testbench

```
|process
|begin
|wait for 100ns;
|cloop: loop
|  Clk<='0';
|  wait for (period/2) ;
|  Clk<='1';
|  wait for (period/2) ;
|end loop;
|end process;

|process
|  file test_vector
|  : text open read_mode is "Instr.txt";
|  variable row
|  : line;
|  variable address
|  : integer;
|  variable instr_data
|  : std_logic_vector(15 downto 0);

|begin
|  wait for 500ns;
|  wait for (5*period) ;

|while( not endfile(test_vector)) loop
|  readline(test_vector,row);
|  read(row,address);
|  read(row,instr_data);
|  Im_WA<=std_logic_vector(to_unsigned(address, Im_WA'length));
|  Im_WD<=instr_data;
|  Im_WE<='1';
|  wait for (2*period) ;
|end loop;
```

```
Im_WA<="000000000000";
Im_WD<="x"0000";
Im_WE<-'0';
wait for (2*period);
wait for (period/2- setup);
Rst<='0';
wait for 100 ns;
interrupt<='1';
wait for 3 ns;
interrupt<='0';
wait ;

end process;

end Behavioral;
```

# Timing Simulation Results

## Interrupt servicing and Return


Name	Value
clk	1
interrupt	0
IM_WE	0
rst	0
mem_write_en	0
> instruction[15:0]	8a4c
> Pc_value[9:0]	300
> data_memory_read[7:0]	00
> mem_read_add[7:0]	4c
> mem_write_add[7:0]	4c
> mem_write_data[7:0]	0f
> Im_WA[9:0]	000
> Im_WD[15:0]	0000
period	20000 ps





# Timing Simulation Results
 
## Store and Load Instruction verification



# Timing Simulation Results

## Conditional (JUMPZ) and unconditional JUMP instructions

Name	Value
clk	1
interrupt	0
IM_WE	0
rst	0
mem_write_en	0
> instruction[15:0]	8a4c
> Pc_value[9:0]	008
> data_memory_read[7:0]	00
> mem_read_add[7:0]	4c
> mem_write_add[7:0]	4c
> mem_write_data[7:0]	02
> Im_WA[3:0]	000
> Im_WD[15:0]	0000
period	20000 ps



# Resource Utilization

## Resource Utilization including Data Memory and Instruction Memory

Resource	Utilization	Available	Utilization %
LUT		617	20800
LUTRAM		416	9600
FF		82	41600
IO		89	106
			83.96

## Individual Resource utilization

Name	^1	Slice LUTs (20800)	Slice Registers (41600)	F7 Muxes (16300)	F8 Muxes (8150)	Bonded IOB (106)	BUFGCTRL (32)
✓ N RISC_Main		617	82	32	16	89	2
> [I] U1 (Data_Mem)		60	8	0	0	0	0
> [I] U2 (Instr_Mem)		432	43	32	16	0	0
✓ [I] U3 (RISC_CPU)		125	31	0	0	0	0
[I] uut1 (Interrupt_Synchr)		2	4	0	0	0	0
[I] uut2 (Controller_and_decoder)		38	5	0	0	0	0
✓ [I] uut3 (data_path)		85	22	0	0	0	0
[I] uut1 (Program_Counter)		14	20	0	0	0	0
[I] uut2 (Register_File)		70	0	0	0	0	0
[I] uut4 (ALU_unit)		1	2	0	0	0	0



# Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 9.615 ns	Worst Hold Slack (WHS): 0.007 ns	Worst Pulse Width Slack (WPWS): 8.750 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 3330	Total Number of Endpoints: 3330	Total Number of Endpoints: 516

All user specified timing constraints are met.

Clock Constraint given 50MHz

Maximum clock frequency= 96.29MHz